



Department of Electrical and Computer Engineering

Circuit Analysis – ENEE2304

PSpice Assignment


Name: Rahaf Naser

ID: 1201319

Section: 1


Question # 1: Superposition Technique

For the circuit shown below:

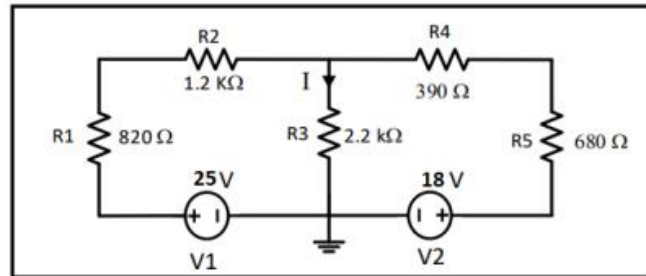

1. Use Pspice software to simulate the circuit and get the voltage across and the current through the resistor R3.

1.

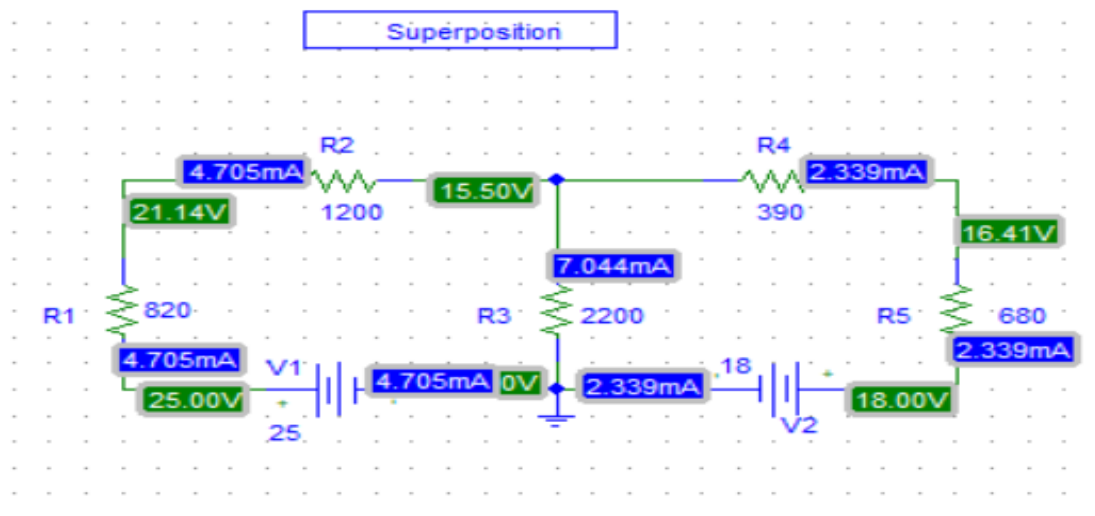


-After simulate the circuit we find that:

1)Voltage across R3 = 15.50 V

2)Current through R3 = 7.044 mA

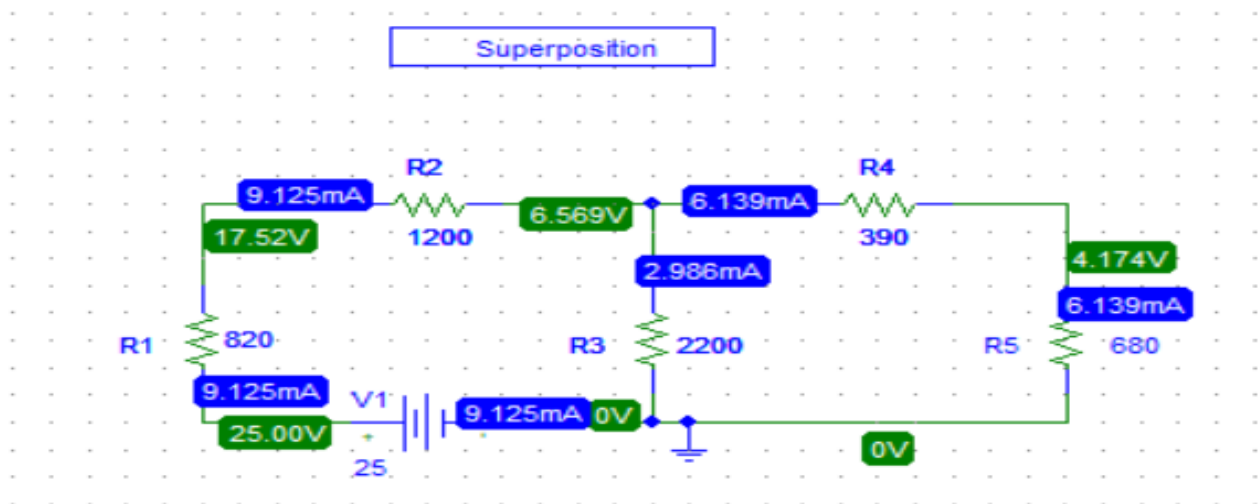2. Apply superposition theorem to get the voltage across and the current through the resistor R3. You have to show all the results of simulation.

-The first step is to replace the second source with short circuit and then find the current and voltage across R3.




- After simulate circuit we find that:

1) $V_{o1} = 6.569 \text{ V}$

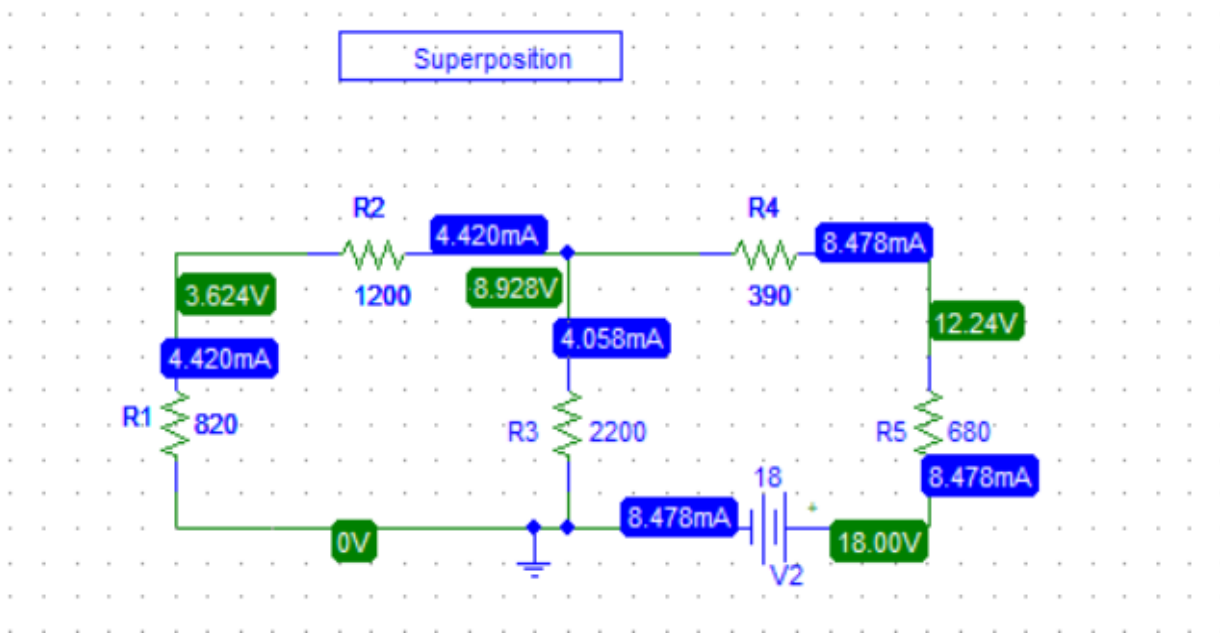2) $I_{o1} = 2.986 \text{ mA}$

-The second step is to replace the first source with short circuit and then find the current and voltage across R3.



- After simulate circuit we find that:

1) $V_{o2} = 8.928 \text{ V}$

2) $I_{o2} = 4.058 \text{ mA}$

-By superposition theorem :

1)Voltage across R3= $V_{o1}+V_{o2}$

$$V=6.569+8.928$$

$$V = 15.50 \text{ V}$$

2)Current through R3= $I_{o1}+I_{o2}$

$$I=2.986+4.058$$

$$I=7.044 \text{ mA}$$

3. Compare the results obtained from step 1 and step 2.

The results that obtained from step1


are equal to the results from step2

voltage across R3 = 15.50 V


current through R3 = 7.044 mA

Question #2: Thevenin's Theorem & Maximum Power Transfer

For the circuit shown below:

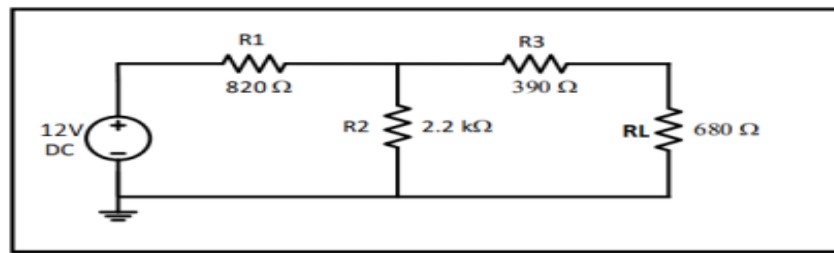

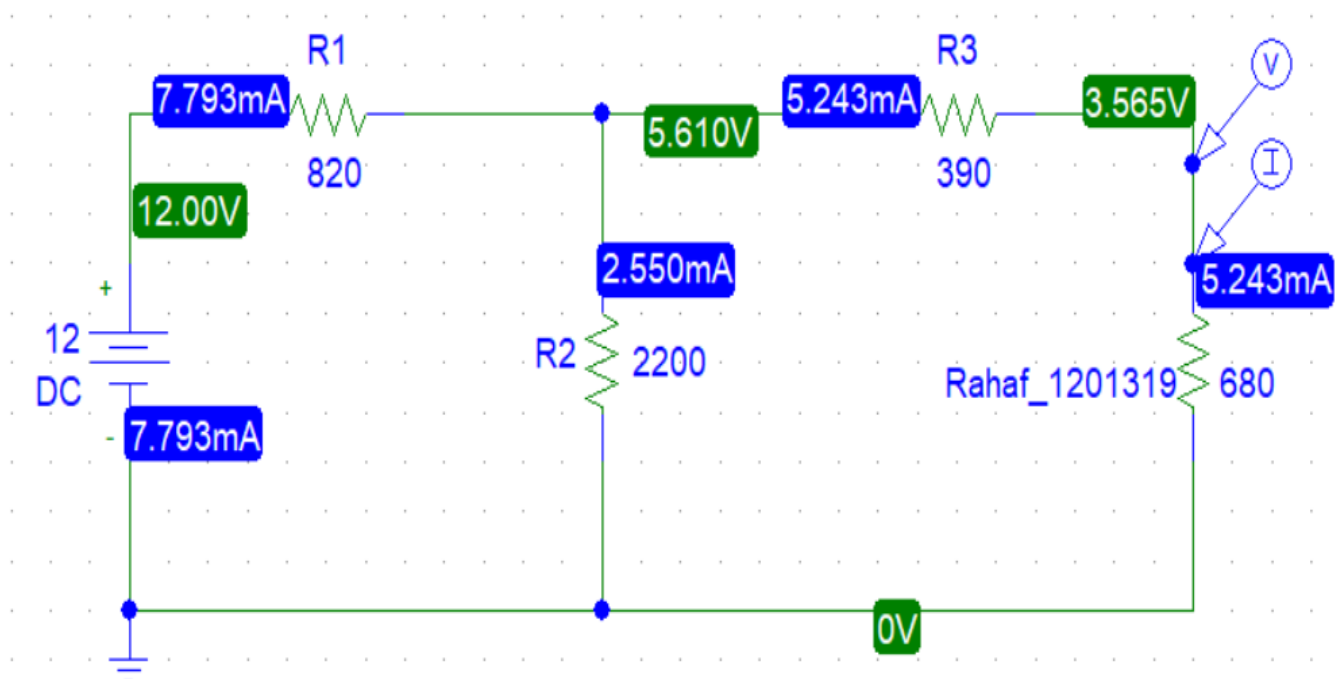1. Use Pspice software to simulate this circuit and get the voltage across and the current through the resistor RL (680 Ω).





-The voltage across RL= 3.565 V

-The current through RL = 5.243 mA

2. Using DC sweep, set R_L as a parameter that varies from $100\ \Omega$ to $1.5\ \text{k}\Omega$ and **plot** the power dissipated by R_L as it varies (plot the power of R_L versus the value of R_L). With the help of cursors on Pspice simulation window, approximate at which value of R_L the power maximizes)

The circuit:

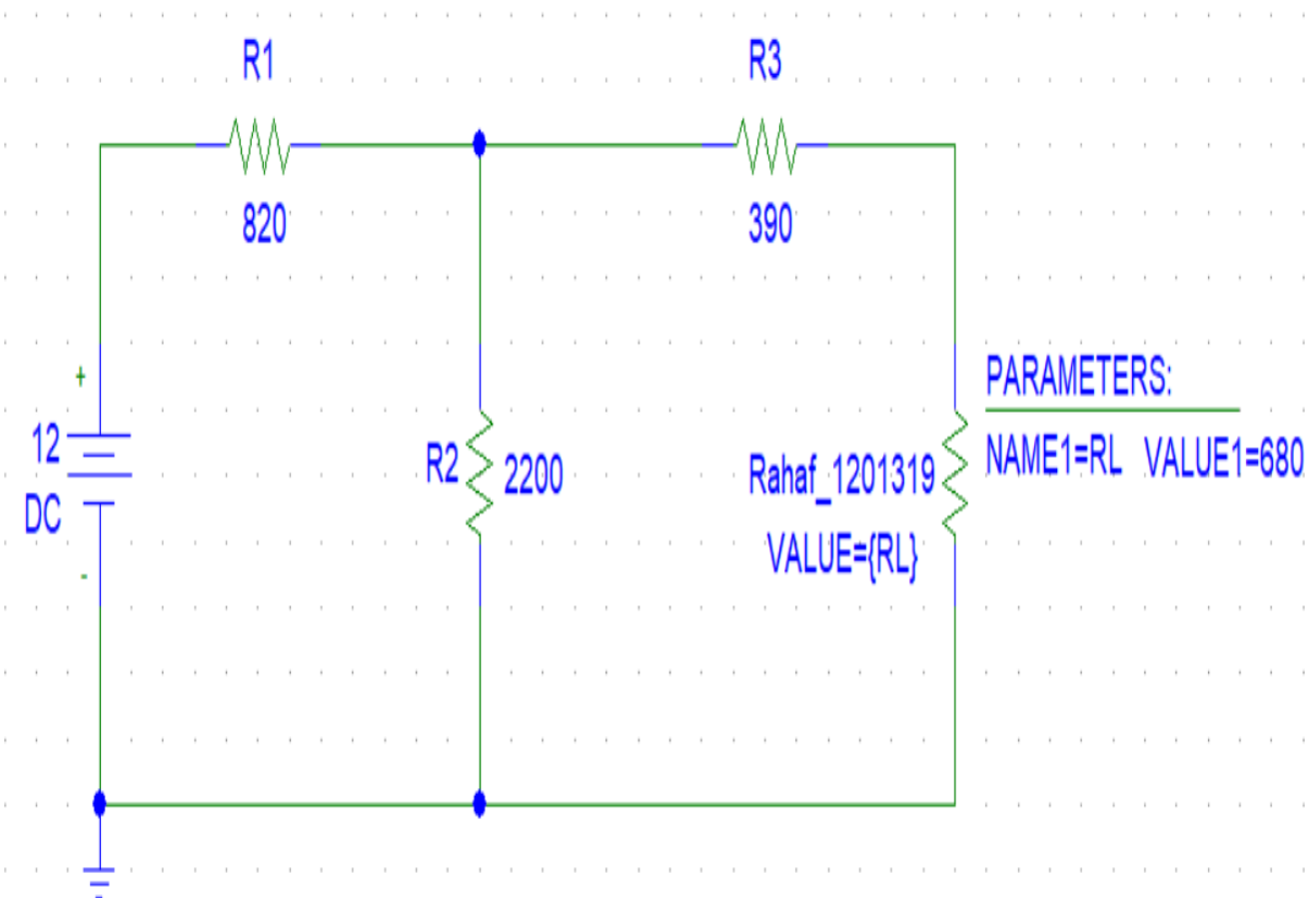

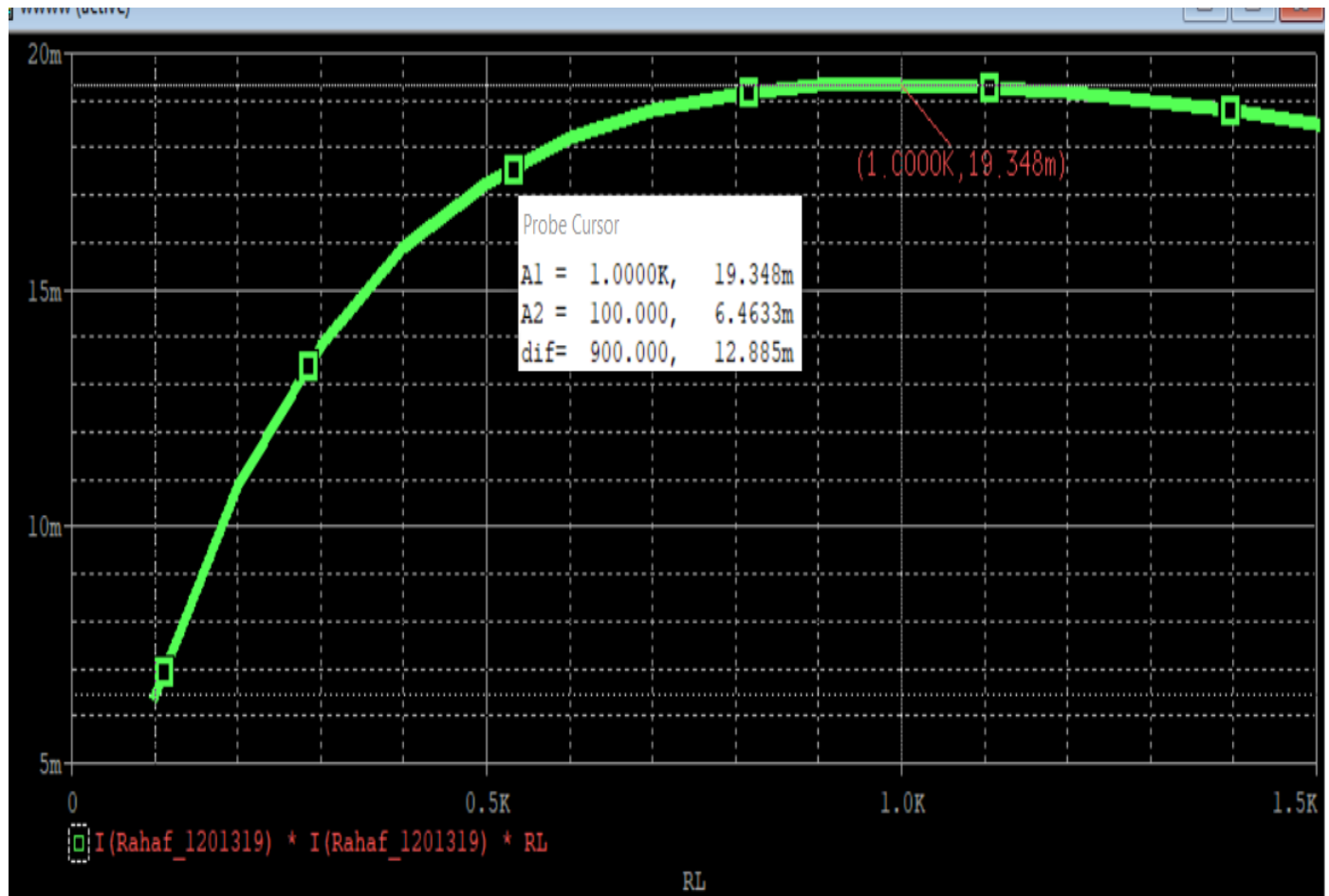


Plot the power of RL versus the value of RL.


The maximum power=19.348 mW

At RL = 1 K ohm

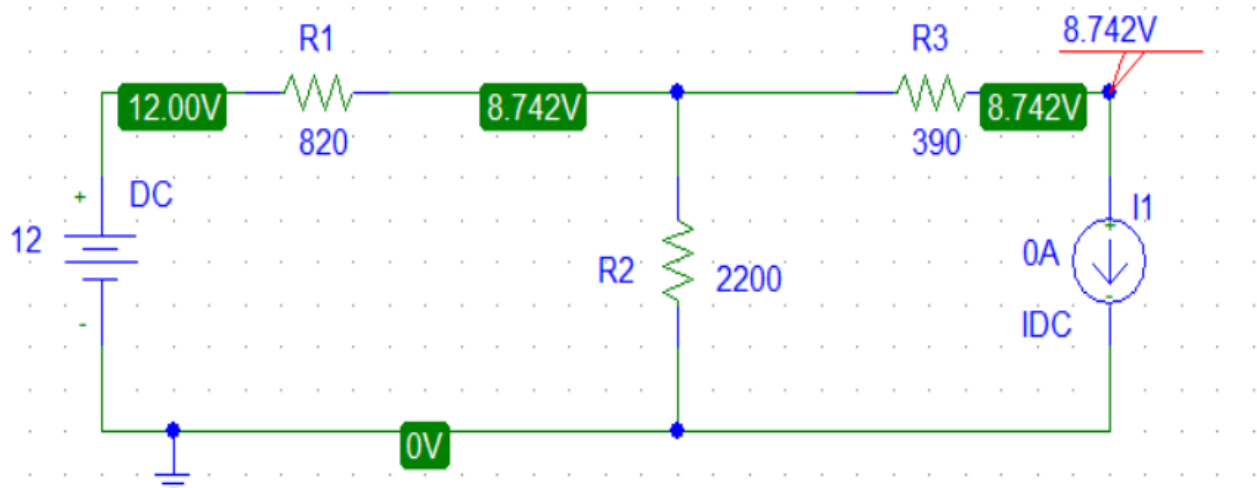3. Use Pspice software to calculate R_{thevenin} seen by the resistor R_L . Use V_{oc} and I_{sc} **method only**. You have to show all the simulation results when getting V_{oc} and I_{sc} .



$$V_{\text{TH}} = 8.742 \text{ V}$$

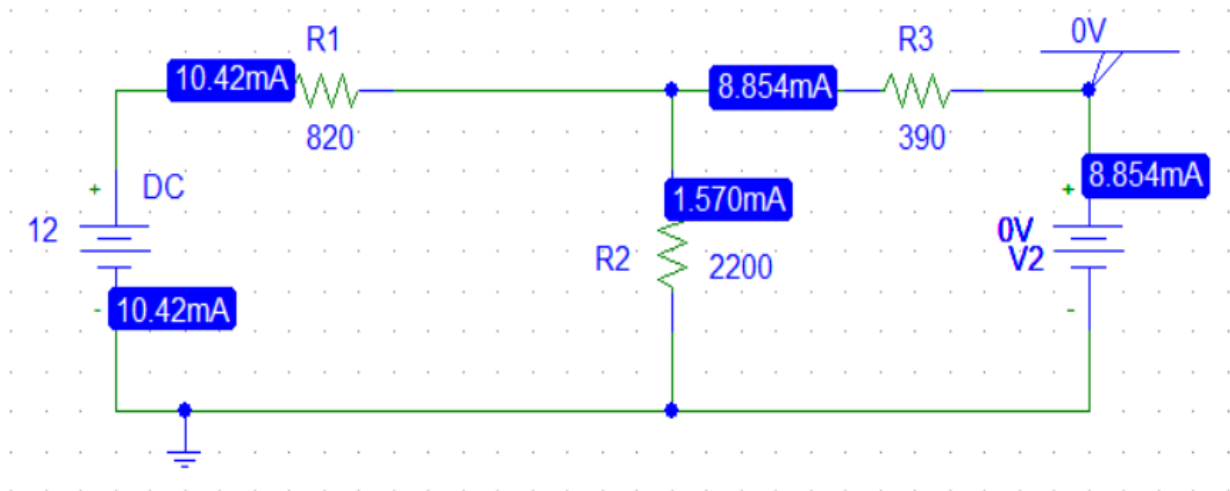

$I_{\text{short circuit}} = 8.854 \text{ mA}$

$$R_{\text{TH}} = V_{\text{TH}} / I_{\text{short circuit}}$$

$$R_{\text{TH}} = 8.742 \text{ V} / 8.854 \text{ mA} = 990 \text{ ohm}$$


4. Compare the value of R_L at P_{\max} obtained from step 2 and the value of R_{thevenin} obtained from step 3.

- R_L at maximum Power = 1000 ohm

- $R_{\text{Thevenin}} = 990$ ohm

The result is $R_L = R_{\text{TH}}$

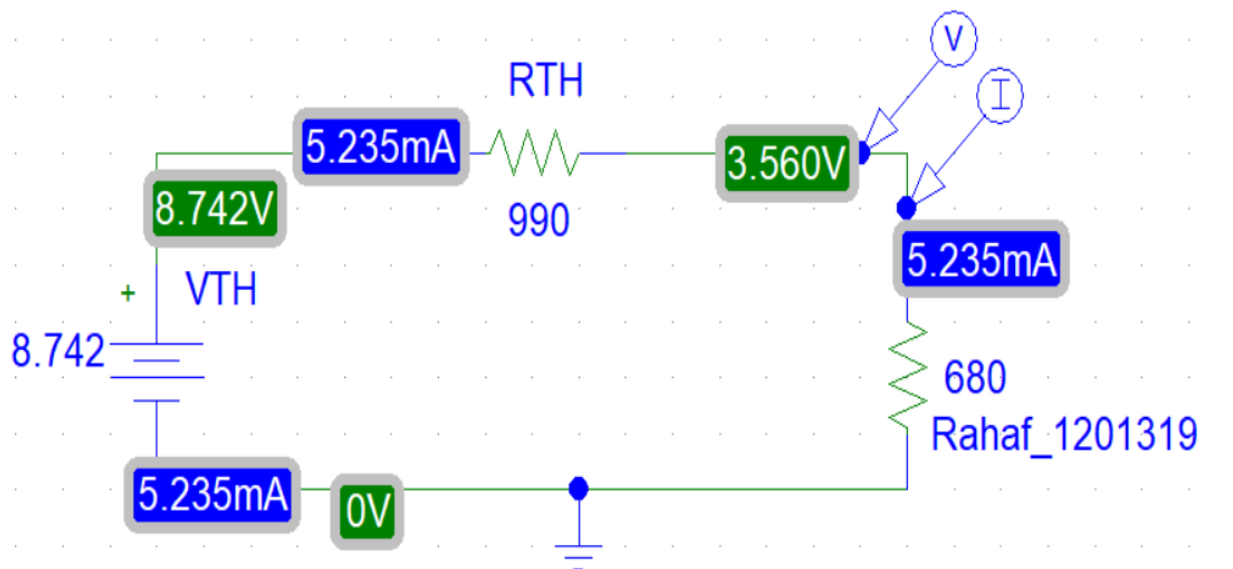5. Build and then simulate the Thevenin equivalent circuit with the load resistor R_L and show the voltage across and the current through the resistor R_L .



*Voltage across $R_L = 3.560\text{v}$

*Current through $R_L = 5.235\text{ mA}$

6. Compare the results obtained from step 1 and step 5.

1- The result of the step 1 is:

*The voltage across $R_L = 3.565 \text{ V}$

*The current through $R_L = 5.243 \text{ mA}$

2- The result of step 5 is:


*Voltage across $R_L = 3.560 \text{ v}$

* Current through $R_L = 5.235 \text{ mA}$

The results are almost equal

Question #3: First Order RC Circuit Analysis


For the circuit shown below:

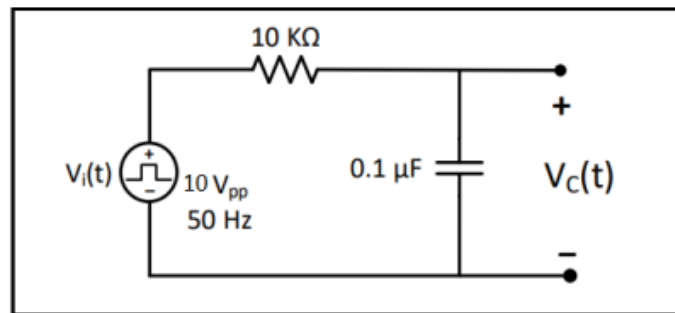


The input voltage is square signal with 10 V peak-peak (0 V to 10 V) and frequency of 50 Hz .


1. Use Pspice software to plot both $V_i(t)$ and $V_C(t)$ (on the same graph) for a meaningful period of time.

The Circuit:

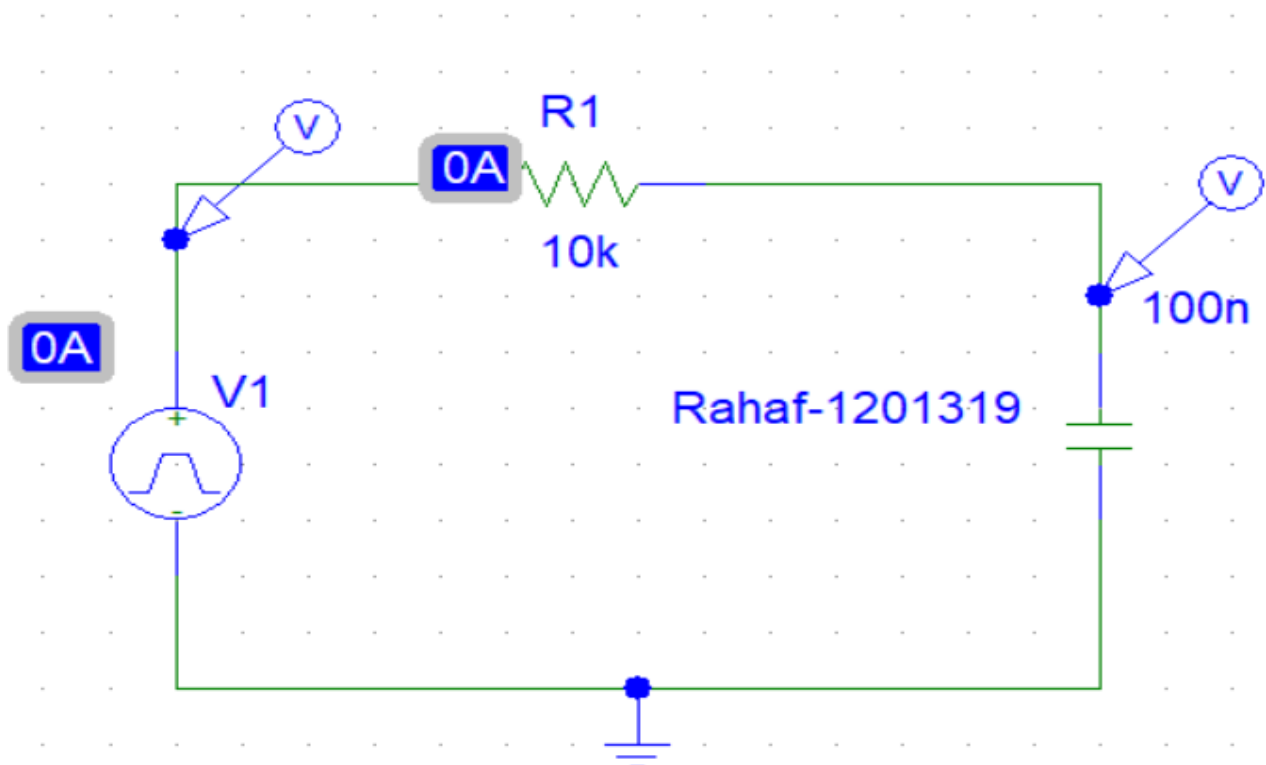

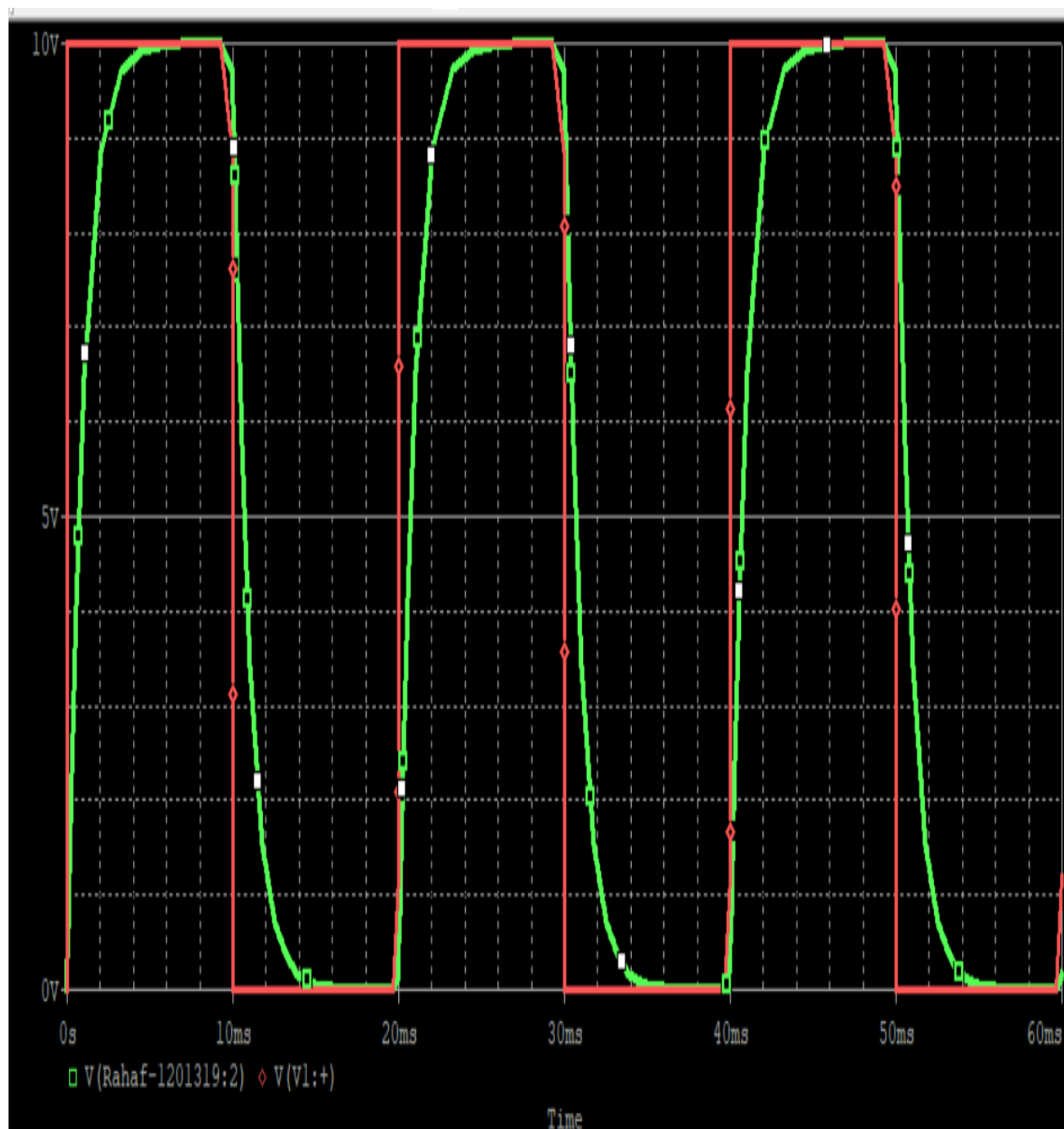

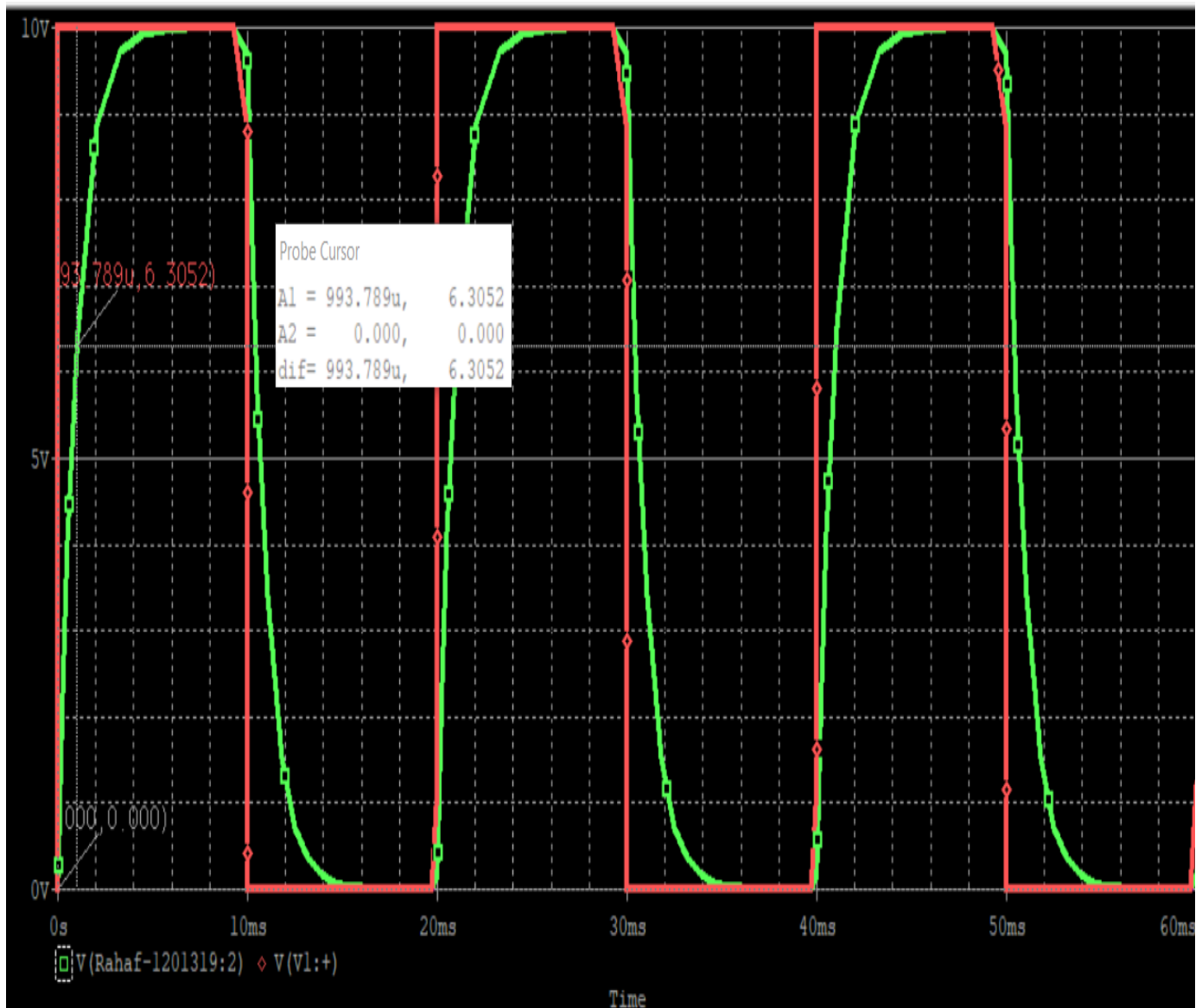2. With help of cursors on Pspice simulation window, show the value of the time constant (τ). You have to show both the circuit and the simulation result.



$$\rightarrow T = R * C = 10000 * 0.1$$

$$\rightarrow = 1 \text{ msec}$$

From the graph:

$$\rightarrow V_{\text{max}} = 10 \text{ volt}$$

$$\rightarrow 0.63 * 10 = 6.3 \text{ volt}$$


By using cursor I find
that when:

$$v = 6.3 \rightarrow T = 0.994 \text{ msec}$$

\rightarrow time constant almost equal 1 msec


Question #4: Second Order RLC Circuit Analysis


For the circuit shown below:

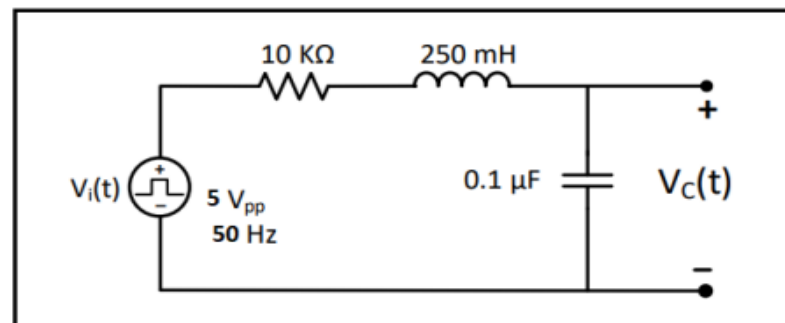

The input voltage is square signal with 5 V peak-peak (0 V to 5 V) and frequency of 50Hz.


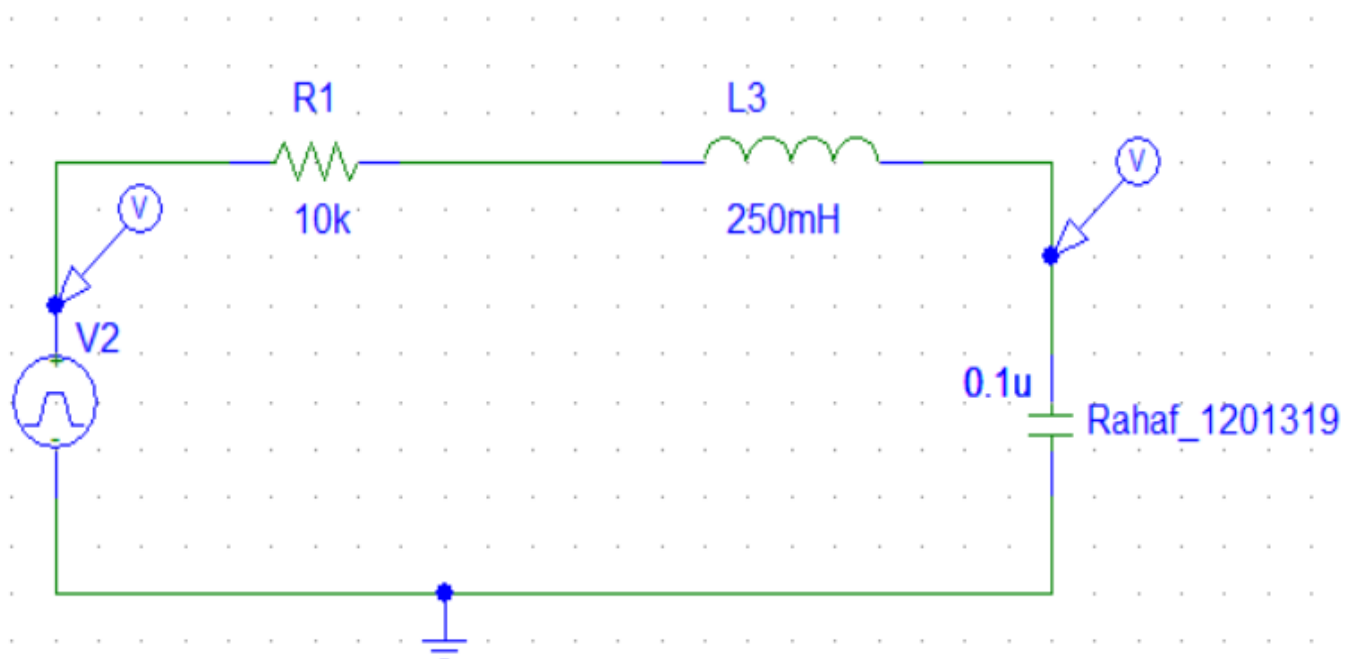
1. Use Pspice software to plot both $V_i(t)$ and $V_C(t)$ (on the same graph).



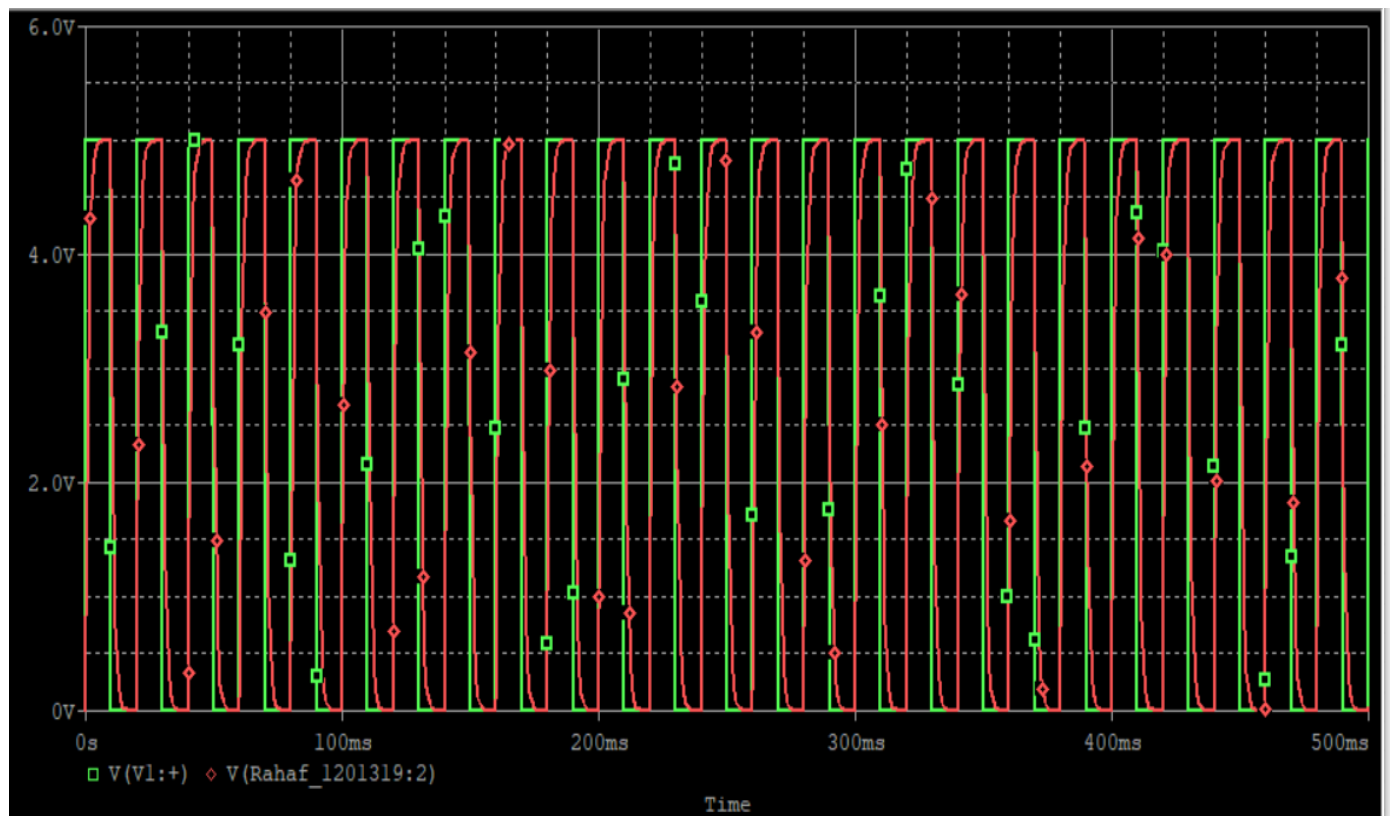



-Over damping response

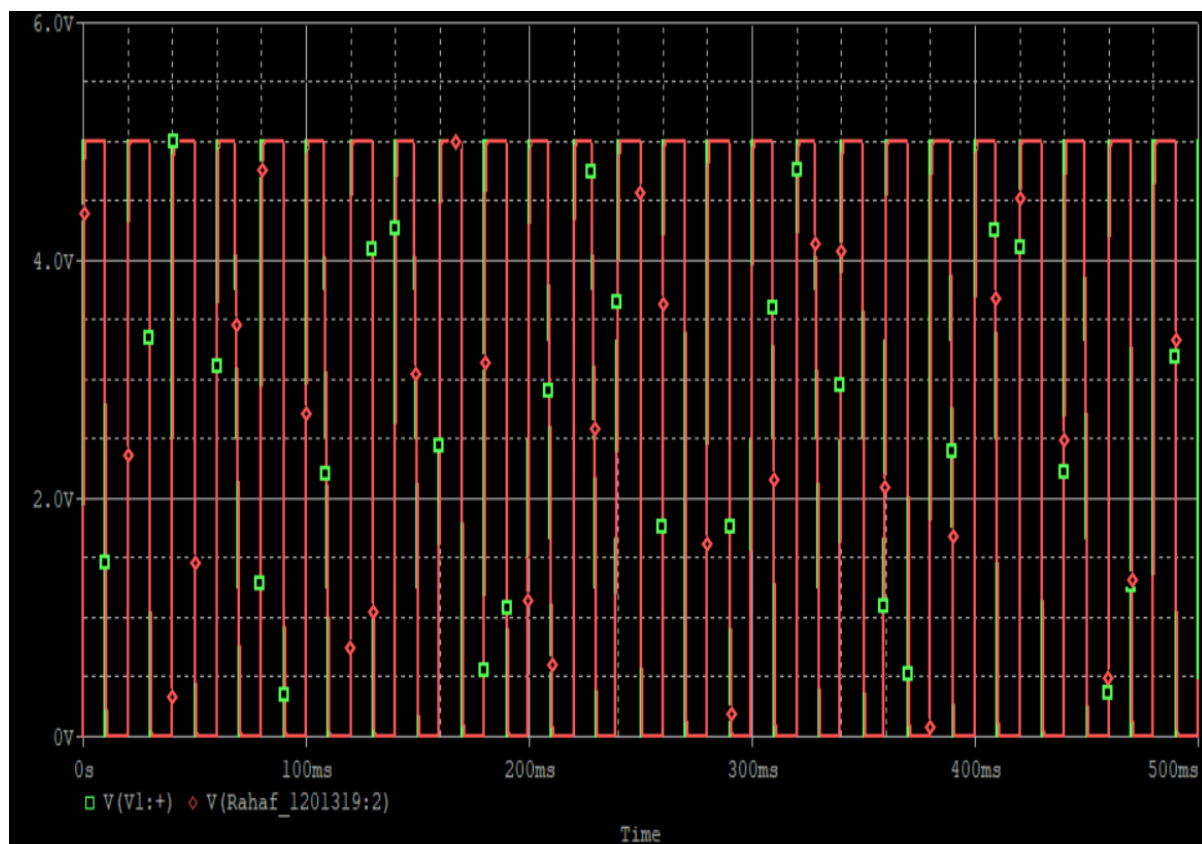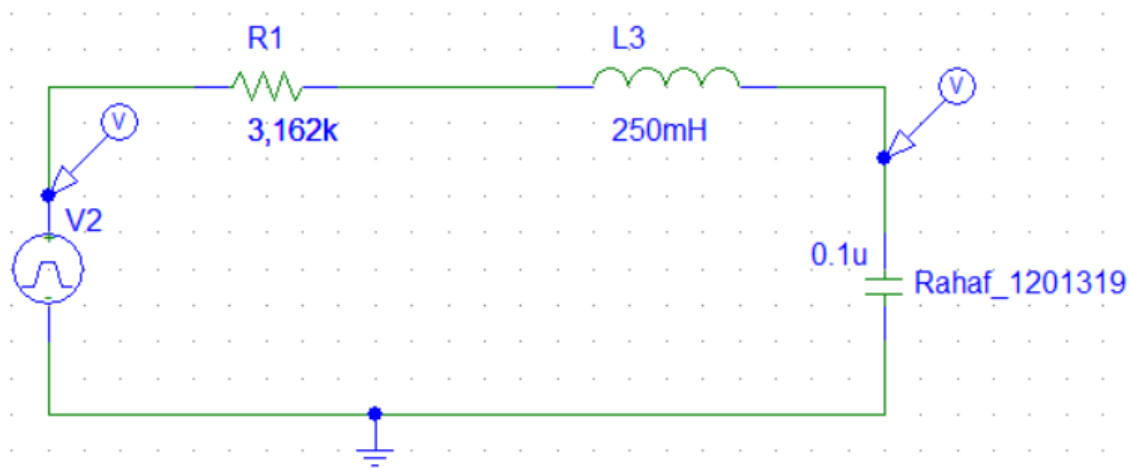2. Change the Value of R to 3.162 k Ω , repeat step 1.



-Critical damping response

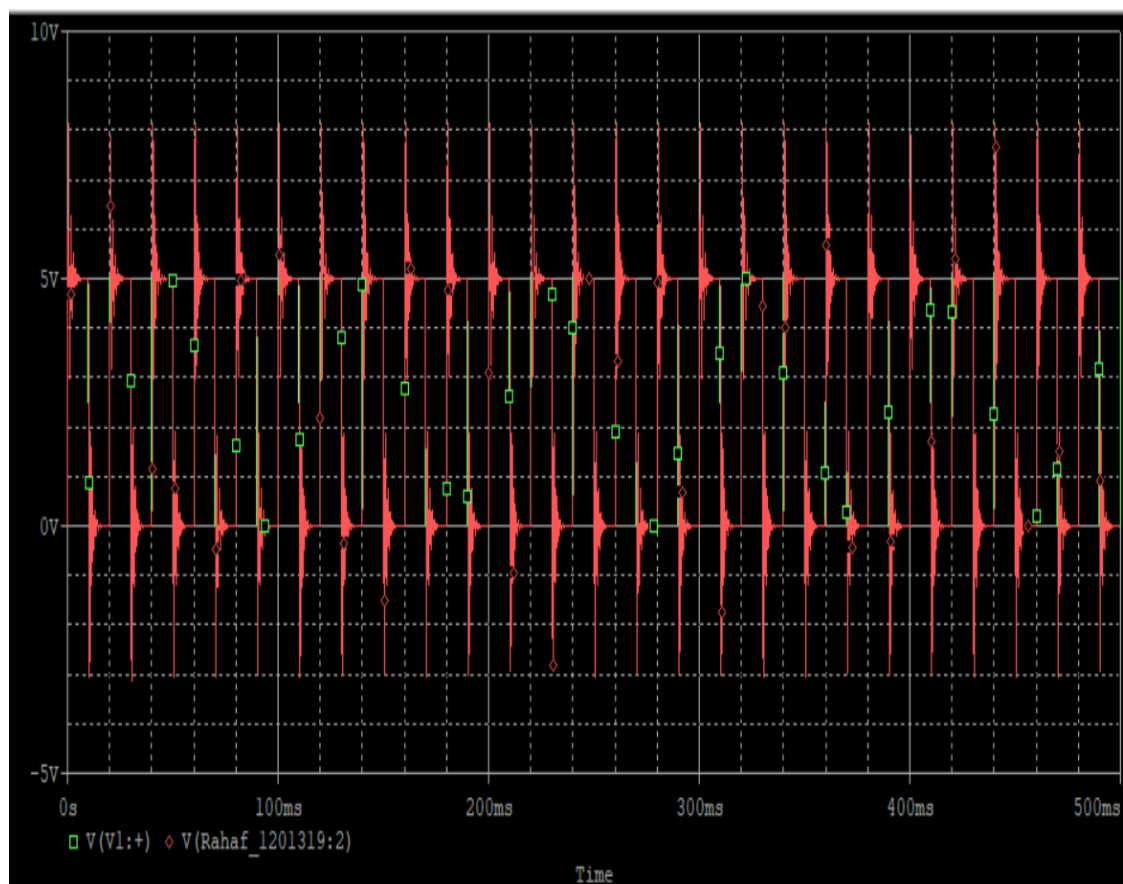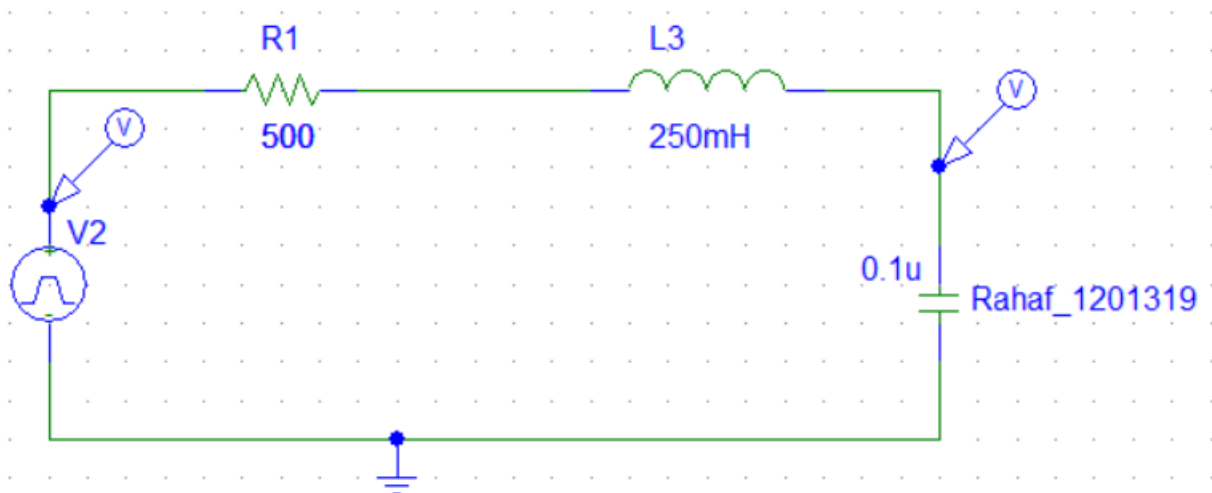3. Change the Value of R to $500\ \Omega$, repeat step 1.



-Under damping response

4. Comment on each result: is it over-damping, critical-damping, or under-damping response.

* RLC circuit can be modeled by

This 2nd-order linear differential equations

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$

The characteristic equation is

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

$$s = \frac{-R \pm \sqrt{R^2 - 4LC}}{2L}$$

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\text{where } \alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

* when $\alpha > \omega_0$ overdamped response

* when $\alpha = \omega_0$ critically damped response

* when $\alpha < \omega_0$ underdamped response

$$\alpha = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0 = \frac{1}{\sqrt{250 \times 10^{-3} \times 2,5 \times 10^{-8}}} = 6329,1$$

a) when $R = 10k\Omega$

$$\alpha = \frac{10 \times 10^3}{2 \times 250 \times 10^{-3}} = 20000$$

$\alpha > \omega_0$ overdamping response

b) when $R = 3,162k\Omega$

$$\alpha = \frac{3,162 \times 10^3}{2 \times 250 \times 10^{-3}} = 6324$$

$\alpha = \omega_0$ critically damping response

c) when $R = 500\Omega$

$$\alpha = \frac{500}{2 \times 250 \times 10^{-3}} = 1000$$

$\alpha < \omega_0$ underdamping response.